

## # Alternating Current (AC):

AC is a periodic current whose average value over a period is zero.



## # Periodic Current (PC):

square wave





An oscillating current which reoccurs at a certain time.


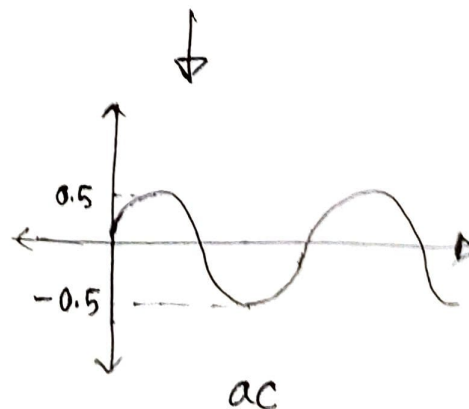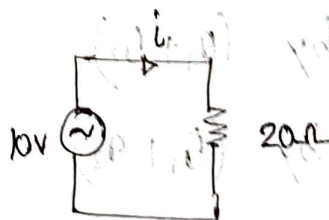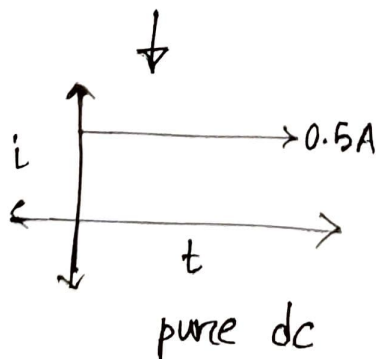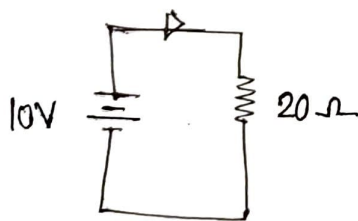
## # Oscillating Current:


pulsating dc

Alternately increases and decreases at definite law.




→ AC can be represented by sine waves.

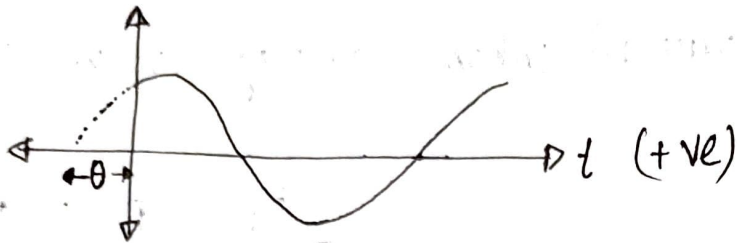→ Smallest recurring values →  $T$  (period)



$$i_1 = I_m \sin(\omega t + \theta_1)$$

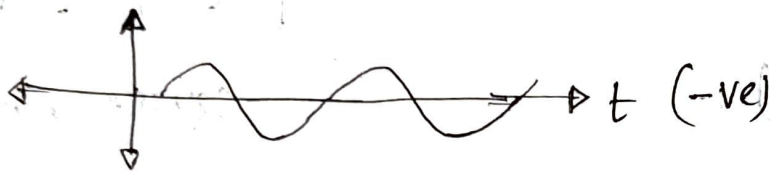

$$i_2 = I_m \sin(\omega t - \theta_2)$$

$$\text{phase difference} = \theta_1 - (-\theta_2) = \theta_1 + \theta_2$$

**Phase** is the fractional part of the period through which time or associated time angle has advanced from an arbitrary reference.


$i_1$  leads  $i_2$  by  $(\theta_1 + \theta_2)$ .

$i_2$  lags  $i_1$  by  $(\theta_1 + \theta_2)$ .

$$\theta_1 - \theta_2 = +ve \quad i_1 \text{ leading, } i_2 \text{ lagging}$$

$$\theta_1 - \theta_2 = -ve \quad i_1 \text{ lagging, } i_2 \text{ leading}$$

### # Impedance function or Impedance :

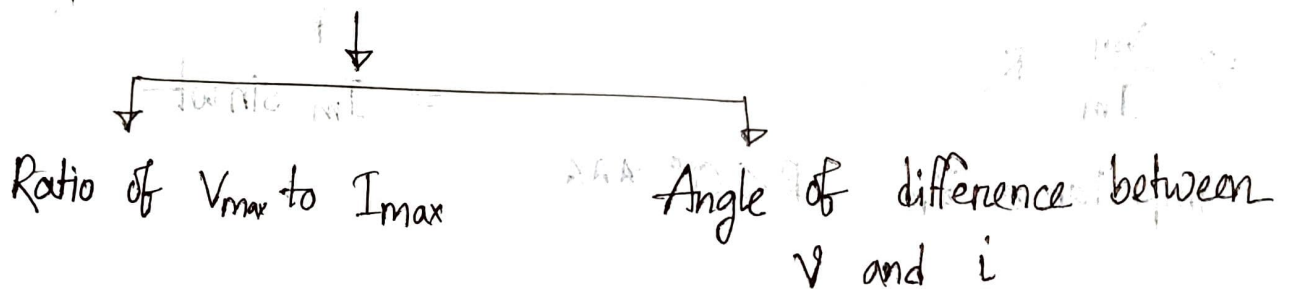


$$\rightarrow \text{impedance } Z \angle \text{Angle} = \frac{V_{\max}}{I_{\max}} \angle \theta_v - \theta_i$$

example :  $v = 150 \sin(\omega t + 75^\circ)$

$$i = 10 \sin(\omega t + 30^\circ)$$

$$\begin{aligned} \therefore \text{impedance } Z \angle \text{Angle} &= \frac{150}{10} \angle (75 - 30)^\circ \\ &= 15 \angle 45^\circ \end{aligned}$$

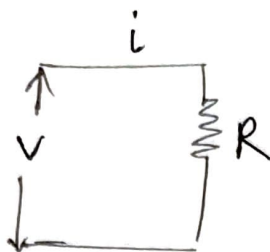parameters : R (resistance), L (inductance),  
C (capacitance), f (frequency).



The R branch: Let  $v = V_{\max} \sin \omega t$  is applied to an

R branch. we know,  $v = iR \Rightarrow i = \frac{v}{R}$

$$\Rightarrow i = \frac{V_m \sin \omega t}{R}$$

$$\Rightarrow \frac{V_m}{I_m} = R$$

$$= I_m \sin \omega t$$

impedance  $Z_R = R \angle 0^\circ$  \*\*\*

example:  $V = 100 \sin(\omega t + 30^\circ)$

$$i = 20 \sin(\omega t + 30^\circ)$$

$$Z = 5 \angle 0^\circ \rightarrow R \text{ Branch}$$


$$\therefore R = 5$$

$$\rightarrow P = vi = V_m I_m \sin^2 \omega t$$

$$= \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$

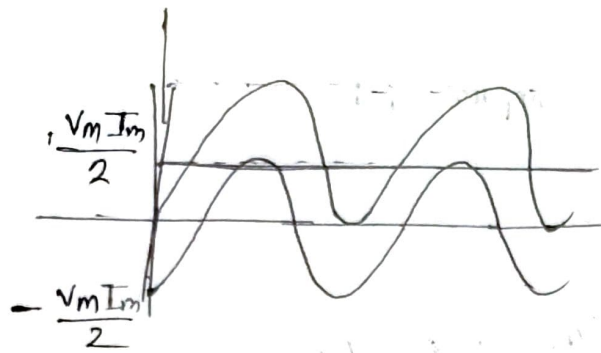$\therefore$  In Resistive Branch  $\rightarrow$  power will always be lost




$$P_{av} = \frac{V_m I_m}{2}$$

Lecture 3  
05.02.2020

$$Z = 5 < 0^\circ$$

যেহেতু,  $\theta_v - \theta_i = 0^\circ$ . সুতরাং, impedance  $\Rightarrow$  resistance

The L Branch :

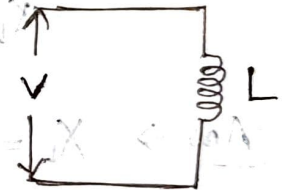

$$V = L \frac{di}{dt} = V_m \sin \omega t$$

$$\Rightarrow \frac{di}{dt} = \frac{V_m}{L} \sin \omega t$$

$$\Rightarrow i = \frac{-V_m}{\omega L} \cos \omega t + C_1 \quad (\text{on integration})$$

↓  
transient current

At steady state value,  $C_1 = 0$

$$i = -\frac{V_m}{\omega L} \cos \omega t = \frac{V_m}{\omega L} \sin(\omega t - 90^\circ)$$



$i = I_m \sin \omega t$  - अब आपसे compare करें,

$$I_m = \frac{V_m}{\omega L}$$

$$\begin{aligned} \therefore \text{impedance, } Z_L &= \frac{V_m}{I_m} < \theta_v - \theta_i \\ &= \omega L < 0 - (-90^\circ) \\ &= \omega L < 90^\circ \quad \star \star \star \end{aligned}$$

inductance reactance,  $X_L = \omega L$

Here,  $L$  is in 'henry'

$X_L = \omega L$  is in 'ohm ( $\Omega$ )'.

example:  $f = 60 \text{ Hz}$ ,

$$L = 10 \times 10^{-3} \text{ H}$$

$$X_L = ?$$

Ans  $\Rightarrow X_L = \omega L$

$$= 2\pi f \cdot L$$

$$= (2\pi \times 60 \times 10 \times 10^{-3}) \Omega$$

$$=$$

#  $V_m = 100 \text{ V}$ ,  $v = ?$   $i = ?$

Ans  $\Rightarrow v = V_m \sin \omega t$

$$= 100 \sin(2\pi \times 60 t)$$

$$i = \frac{V_m}{\omega L} \sin(\omega t - 90) = \frac{100}{2\pi \times 60 \times 10 \times 10^{-3}} \sin(2\pi \times 60 t - 90)$$

(Ans)

$$\# \quad p = vi$$


$$= (V_m \sin \omega t) \cdot \{I_m \sin (\omega t - 90^\circ)\}$$

$$= -\frac{V_m I_m}{2} \sin 2\omega t$$

$$P_{avg} = 0$$

Here,  $v$  and  $i$  waves are single frequency variation but  $p$  double frequency variation.


There is no loss in pure inductance.

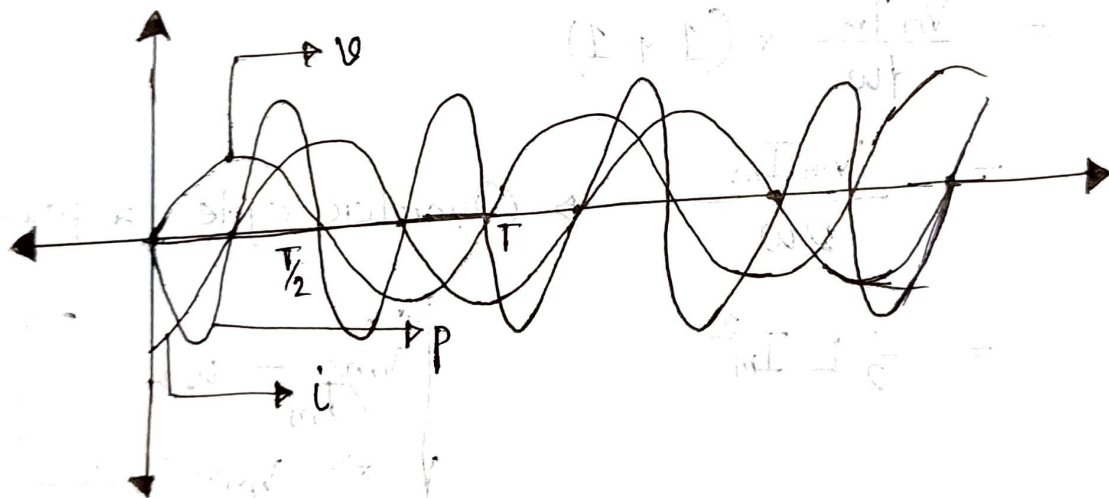

Time period  $\rightarrow$  half of  $v$  or  $i$  wave.

$$\begin{aligned}
 P &= \int_{T/4}^{T/2} -\frac{V_m I_m}{2} \sin 2\omega t \, dt \\
 &= \left[ -\frac{V_m I_m}{2} (-\cos 2\omega t) \cdot \frac{1}{2\omega} \right]_{T/4}^{T/2} \\
 &= \frac{V_m I_m}{4\omega} \left\{ \cos 2 \cdot \frac{2\pi}{T} \cdot \frac{T}{2} - \cos 2 \cdot \frac{2\pi}{T} \cdot \frac{T}{4} \right\} \\
 &= \frac{V_m I_m}{4\omega} \{ \cos 2\pi - \cos \pi \} \\
 &= \frac{V_m I_m}{4\omega} \times (1 + 1) \\
 &\Rightarrow \frac{V_m I_m}{2\omega} \rightarrow \text{Quarter cycle power} \\
 &= \frac{1}{2} L I_m^2 \quad \left[ \begin{array}{l} V_m/I_m = \omega L \\ \Rightarrow V_m = I_m \omega L \end{array} \right]
 \end{aligned}$$

Capacitance :

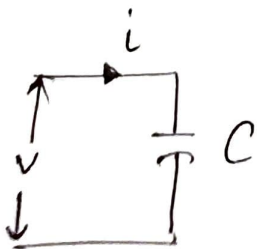

$$\begin{aligned}
 v &= \frac{q}{C} = V_m \sin \omega t \\
 \Rightarrow e &= \frac{q}{V_m} \quad q = V_m C \sin \omega t \\
 i &= \frac{dq}{dt} = V_m \omega C \cos \omega t \\
 &= \frac{V_m}{\frac{1}{\omega C}} \sin(\omega t + 90^\circ)
 \end{aligned}$$



$$i = I_m \sin(\omega t + 90^\circ)$$

$$\therefore I_m = \frac{V_m}{\frac{1}{\omega C}}$$

$$\Rightarrow \frac{V_m}{I_m} = \frac{1}{\omega C}$$

impedance,  $Z_c = \left( \frac{1}{\omega C} \right) < -90^\circ$  \*\*\*

capacitive reactance  $X_c = \frac{1}{\omega C}$

Here,  $C$  is in Farade (F)

$\frac{1}{\omega C}$  is in ohm ( $\Omega$ )

example:  $f = 25 \text{ Hz}$ ,  $C = 15 \text{ MF}$ ,  $X_c = ?$ ,  $V_m = 200 \text{ V}$

$$X_c = \frac{1}{\omega C}$$

$$= \frac{1}{2\pi f \times C} = \frac{1}{2 \times 3.1416 \times 25 \times 15 \times 10^{-6}} = 424.41 \Omega$$

(Ans)

$$i = \frac{V_m}{\frac{1}{\omega C}} \sin(\omega t + 90^\circ)$$

$$= 0.471 \sin(157.08t + 90^\circ) \quad (\text{Ans})$$

$$P = v i = V_m \sin \omega t \cdot I_m \sin(\omega t + 90^\circ)$$


$$= 200 \times 0.471 \sin(157.08t) \cdot \sin(157.08t + 90^\circ)$$

$$= 94.2$$

$$P = vi$$

$$= V_m \sin \omega t \cdot I_m \sin(\omega t + 90^\circ)$$

$$= \frac{V_m I_m}{2} \sin(2\omega t)$$

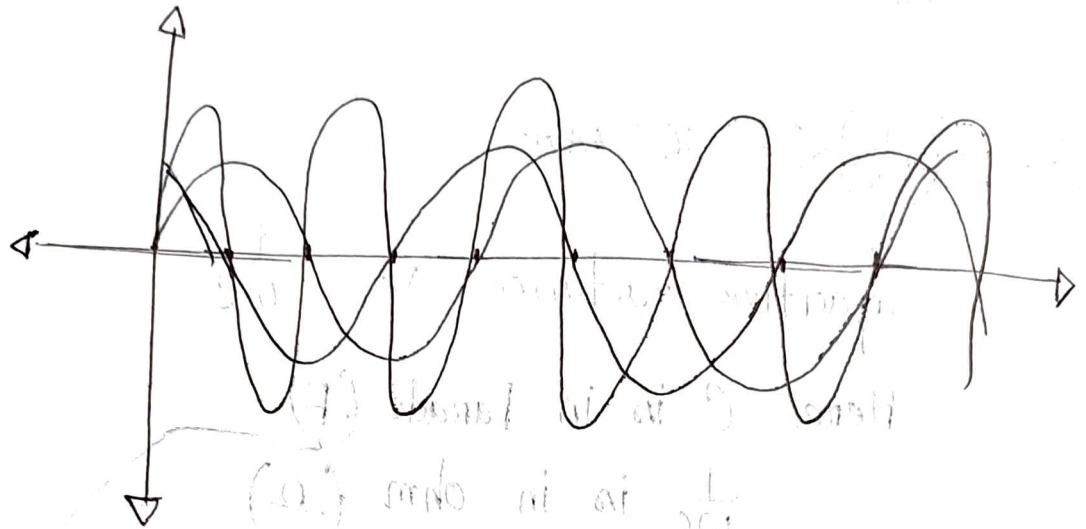



$$W_c = \int_0^{T/4} \frac{V_m I_m}{2} \sin 2\omega t \, dt$$

# R-L Branch:

$$\text{voltage drop, } v = Ri + L \frac{di}{dt}$$

$$\text{Let, } i = I_m \sin \omega t$$
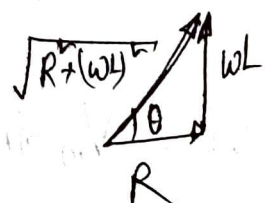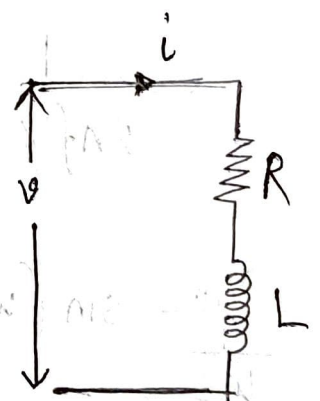
$$\Rightarrow v = R I_m \sin \omega t + \omega L I_m \cos \omega t$$



$$\Rightarrow \frac{v}{\sqrt{R^2 + (\omega L)^2}} = \frac{R}{\sqrt{R^2 + (\omega L)^2}} I_m \sin \omega t + \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}} \cdot I_m \cos \omega t$$

$$\Rightarrow \frac{v}{\sqrt{R^2 + (\omega L)^2}} = I_m \cos \theta \sin \omega t + I_m \sin \theta \cos \omega t$$

$$\Rightarrow \frac{v}{\sqrt{R^2 + (\omega L)^2}} = I_m \sin(\omega t + \theta)$$

$$\Rightarrow v = I_m \cdot \sqrt{R^2 + (\omega L)^2} \sin(\omega t + \theta)$$

$$\Rightarrow v = V_m \sin(\omega t + \theta)$$

$$\therefore \frac{V_m}{I_m} = \sqrt{R^2 + (\omega L)^2}$$

$$\Rightarrow \frac{V_m}{I_m} = \sqrt{R^2 + (\omega L)^2}$$

$$\tan \theta = \frac{\omega L}{R} \Rightarrow \theta = \tan^{-1} \frac{\omega L}{R}$$

$$\text{impedance} = \sqrt{R^2 + (\omega L)^2} < \theta$$

$$\text{of R-L Branch} = \sqrt{R^2 + (\omega L)^2} < \tan^{-1} \frac{\omega L}{R}$$

# Voltage leading,

Current lagging,

ex:  $R = 20 \Omega$   
 $L = 0.056 \text{ Henry}$   
 $f = 60 \text{ Hz}$

$$Z_{RL} = \sqrt{R^2 + (\omega L)^2} < \tan^{-1} \frac{\omega L}{R}$$

$$= 29.08 < 46.55^\circ$$

$$v = 200 \sin 377t,$$

$$i = I_m \sin \omega t \quad V_m = 200$$

$$= 6.88 \sin(376.99t - 46.5) \frac{V_m}{I_m} = \sqrt{R^2 + (\omega L)^2}$$

$$\Rightarrow I_m = 6.88$$

$$i = 6.88 \sin(376.99t - 46.5)$$

#  $P = v i$

$$= \frac{V_m I_m}{2} 2 \sin \omega t \cdot \cos \theta + \frac{V_m I_m}{2} 2 \sin \omega t \cdot \cos \omega t \cdot \sin \theta$$

$$= \frac{V_m I_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos \theta \cdot \cos 2\omega t + \frac{V_m I_m}{2} \sin \theta \cdot \sin 2\omega t$$

$$= \frac{V_m I_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos(2\omega t + \theta)$$

$$P_{avg} = \frac{V_m I_m}{2} \cos \theta \quad (\text{Real Value Power})$$

$$\text{Power : Reactive power} = \frac{V_m I_m}{2} \sin \theta$$

$$\text{Power factor} = \cos \theta$$

$$\text{Reactive factor} = \sin \theta$$

### R-L CKT

$$Z_{R-L} = \sqrt{R^2 + (\omega L)^2} \angle \tan^{-1} \frac{\omega L}{R}$$

$$v = V_m \sin(\omega t + \theta), \quad i = I_m \sin \omega t$$

$$p = vi = \frac{I_m V_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos \theta \cos 2\omega t + \frac{V_m I_m}{2} \sin \theta \sin 2\omega t$$

$$\frac{V_m I_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos \theta \cos 2\omega t \rightarrow \text{Instantaneous Real Power (always +ve)}$$

$$\frac{V_m I_m}{2} \cos \theta \rightarrow \text{Real Power ; Power factor} = \cos \theta \quad (\text{p.f.})$$

$$\frac{V_m I_m}{2} \sin \theta \sin 2\omega t \rightarrow \text{Instantaneous Reactive Power}$$

$$P_{av} = \frac{V_m I_m}{2} \cos \theta \rightarrow \text{measured by a wattmeter.}$$

$$\frac{V_m I_m}{2} \sin \theta \rightarrow \text{Reactive power ; Reactive factor} = \sin \theta \quad (\text{r.f.})$$

↓  
measured by varmeter




## R-L-C Branch :

$$v = Ri + L \frac{di}{dt} + \frac{q}{C}$$

Let,  $i = I_m \sin \omega t$  and
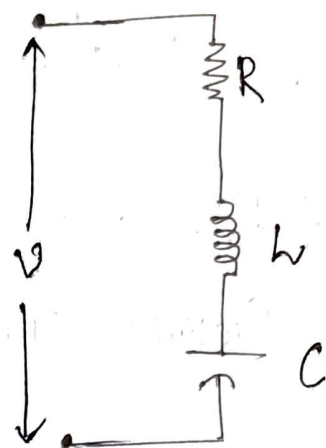
$$\frac{q}{C} = \frac{\int i dt}{C} = \frac{-I_m \cos \omega t}{\omega C}$$




$$\therefore v = RI_m \sin \omega t + \omega L I_m \cos \omega t - \frac{1}{\omega C} I_m \cos \omega t$$

$$= I_m R \sin \omega t + I_m \left( \omega L - \frac{1}{\omega C} \right) \cos \omega t$$

dividing both the sides by  $\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}$
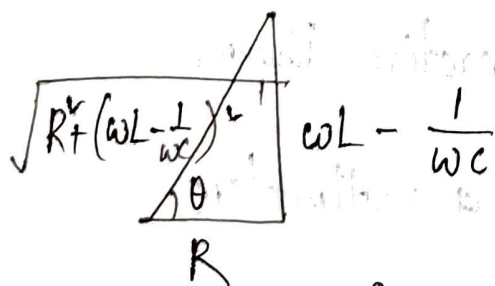
$$\frac{v}{\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}} = I_m \frac{R}{\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}} \sin \omega t + I_m \frac{\left( \omega L - \frac{1}{\omega C} \right)}{\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}} \cos \omega t$$



$$\text{Let } \cos \theta = \frac{R}{\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}}$$

$$\text{then } \sin \theta = \frac{\omega L - \frac{1}{\omega C}}{\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}}$$

$$\Rightarrow v = I_m \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \sin(\omega t + \theta)$$

$$= V_m \sin(\omega t + \theta)$$

$$\text{impedance } Z_{RLC} = \frac{V_m}{I_m} \angle \theta$$

$$= \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \angle \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R}$$

e.g:  $R = 20 \Omega$   $L = 0.056 \text{ henry}$   $C = 50 \mu\text{F}$

$v = 200 \sin 377t$  ,  $Z_{RLC} = ?$   $i = ?$

$$\Rightarrow v = V_m \sin \omega t$$

$$\therefore \omega = 377$$

~~$\Rightarrow$~~   ~~$Z_{RLC}$~~

$$\therefore Z_{RLC} = \sqrt{(20)^2 + \left(377 \times 0.056 - \frac{1}{377 \times 50 \times 10^{-6}}\right)^2} \angle \tan^{-1} \frac{377 \times 0.056 - \frac{1}{377 \times 50 \times 10^{-6}}}{20}$$

$$= 37.68 \angle$$

$$= 33.467 \angle 88.23^\circ \quad 33.467 \angle -72.61^\circ$$

$$i = \frac{200}{33.5} \sin(377t + 72.61^\circ)$$

12.  $v = 100 \sin(\omega t - 30^\circ)$  and  $i = 10 \sin(\omega t - 60^\circ)$

$i$  and  $v = ?$  lead = ?

phase difference

~~$V_m = 100$~~

$v =$

L Ans: phase difference =  $-60 - (-30)$   
 $= -30$

$v$  is leading.

13.  $v = 100 \cos(\omega t - 30^\circ)$  &  $i = -10 \sin(\omega t - 60^\circ)$

phase difference  $v$  &  $i = ?$  lag?

$v = 100 \sin(\pi/2 + \omega t - 30^\circ)$

$= 100 \sin(\omega t + 120^\circ)$

$i = 10 \sin(180^\circ + \omega t - 60^\circ)$

$= 10 \sin(\omega t + 120^\circ)$

$v$  &  $i = \overset{+60}{-120} - (+120) = 0^\circ - 60^\circ$

L  $\therefore v$  lagging.

th

$$18. \quad v = 150 \cos 314t$$

$$R = 30 \Omega$$

$$a) \quad i = ?$$

$$b) \quad f_v = ? \quad f_i = ?$$

$$c) \quad P = ?$$

$$d) \quad f_p = ?$$

$$A: \quad v = 150 \sin(90 + 314t)$$

$$\omega = 314$$

$$\Rightarrow 2\pi f = 314$$

$$\Rightarrow \boxed{f_v = 50 = f_i}$$

$$\frac{I_m}{V_m} = R \quad \frac{V_m}{I_m} = R$$

$$\Rightarrow I_m = \frac{150}{30} A = 5A$$

$$\boxed{i = 5 \cos(314t)}$$

$$\boxed{\therefore f_p = 100}$$

$$P = vi$$


$$= 150 \times 5 \times \cos^2(314t)$$

$$= \boxed{750 \cos^2(314t)} = 375 (1 + \cos 628t)$$

$$= 375 + 375 \cos 628t$$

$$22. \quad v = -150 \sin 377t$$

$$i = 10 \cos 377t$$

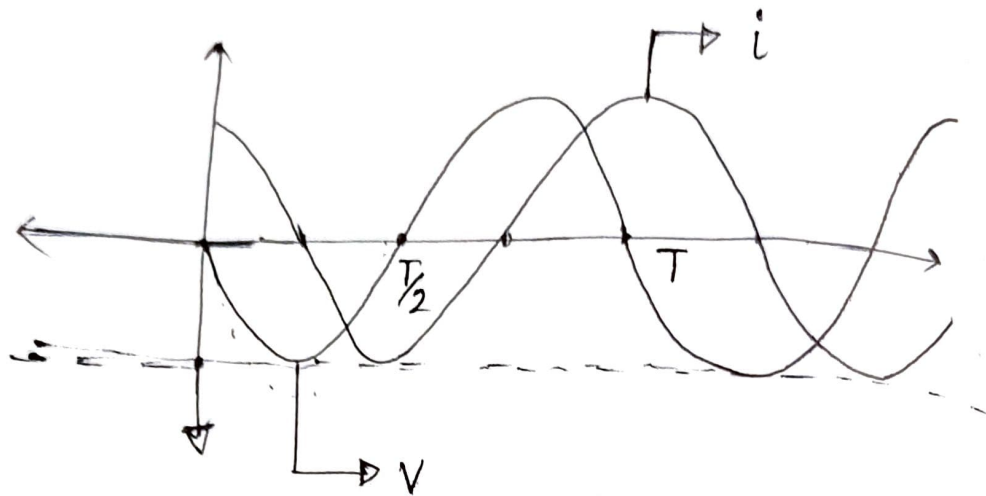

$$v = 150 \sin (180 + 377t)$$

$$i = 100 \sin (90 + 377t)$$

$$\therefore \text{phase difference} = \theta_v - \theta_i = 180^\circ - 90^\circ = 90^\circ$$

$$\frac{1}{\sqrt{R^2 + L^2}}$$

$\therefore v$  leading and  $i$  lagging.

② Nature : Inductance.

$$\sqrt{R^2 + L^2}$$

$$I_m = \frac{V_m}{\omega L}$$

$$\Rightarrow L = \frac{V_m}{I_m \omega} = 0.0397 \text{ henry}$$



29.  $R = 10 \Omega$  ,  $L = 0.05 \text{ henry}$

$f = 25 \text{ cycles}$  ,  $V_m = 150 \text{ V}$

a)  $Z_{R-L} = ?$

b)  $v = 75$  at  $t = 0$  , voltage equation = ?

c)  $i = ?$       d)  $P = ?$

$$\begin{aligned} \text{a) } Z_{R-L} &= \sqrt{R^2 + (\omega L)^2} \angle \tan^{-1} \frac{\omega L}{R} \\ &= \sqrt{10^2 + (2\pi \times 25 \times 0.05)^2} \angle \tan^{-1} \frac{2\pi \times 25 \times 0.05}{10} \\ &= 12.7 \angle 38.14^\circ \end{aligned}$$

b)  $v = V_m \sin(\omega t + \theta_v)$

$= 150 \sin (157t + 30)$

$0 \ 75 = 150 \sin \theta$

$\Rightarrow \theta = 30^\circ$

c)  $i = I_m \sin(\omega t + \theta_i)$

$$\frac{V_m}{I_m} = \sqrt{R^2 + (\omega L)^2}$$

$\Rightarrow I_m = 11.81$

$\theta_v - \theta_i = 38.14 \Rightarrow \theta_i = -8.14 \therefore i = 11.81 (157t - 8.14)$